

به نام خدا

عنوان:

تکلیف شماره دوم درس طراحی سیستم‌های دیجیتال

نام درس:

طراحی سیستم‌های دیجیتال

استاد درس:

دکتر مروستی

اعضا:

محمد علی مجتهد سلیمانی - ۹۹۲۰۲۳۰۳۹

تاریخ:

۱۴۰۳/۰۲/۲۰

Question 1

Q1. For verify a 4-bit carry look-ahead adder we should first make a test bench to simulate all possible inputs and check the outputs against expected values which test bench going to do that. For the following code I assumed that you already have a Carry-Look-Ahead Adder module, for my code I already done it in first homework question 4.

❖ **Main code for implement partial full adder:**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Define the entity for the Partial Full Adder
entity partial_full_adder is
    Port (
        A    : in  STD_LOGIC; -- Input bit A
        B    : in  STD_LOGIC; -- Input bit B
        Cin   : in  STD_LOGIC; -- Carry input
        S     : out STD_LOGIC; -- Sum output
        P     : out STD_LOGIC; -- Propagate output
        G     : out STD_LOGIC; -- Generate output
    );
end partial_full_adder;

-- Architecture declaration using a behavioral model
architecture Behavioral of partial_full_adder is
begin
    -- Generate the Sum (S) output
```

$S \leftarrow A \text{ xor } B \text{ xor } C_{in};$

-- Generate the Propagate (P) output

$P \leftarrow A \text{ or } B;$

-- Generate the Generate (G) output

$G \leftarrow A \text{ and } B;$

end Behavioral;

❖ Complication Report:

The screenshot displays the Quartus II 64-bit IDE interface. The top menu bar includes File, Edit, View, Project, Assignments, Processing, Tools, Window, and Help. The Project Navigator on the left shows the project hierarchy with 'Entity' and 'partial_full_adder'. The main window is divided into three panes: 'Table of Contents', 'Flow Summary', and 'Messages'.

The 'Flow Summary' pane displays the following information:


Flow Summary	Flow Status
Quartus II 64-bit Version	Successful - Fri May 10 21:50:41 2024
Revision Name	13.1.0 Build 162 10/23/2013 SJ Web Edition
Top-level Entity Name	partial_full_adder
Family	Cyclone V
Device	SCGXPC7C7F23C8
Timing Models	Final
Logic utilization (in ALMs)	N/A
Total registers	0
Total pins	6
Total virtual pins	0
Total block memory bits	0
Total DSP Blocks	0
Total HSSI RX PCSs	0
Total HSSI PMA RX Deserializers	0
Total HSSI TX PCSs	0
Total HSSI TX Channels	0
Total PLLs	0
Total DLLs	0

The 'Messages' pane at the bottom shows the following log entries:


- Command: quartus_map --read_settings_files=on --write_settings_files=off partial_full_adder -c partial_full_adder
- 11104 Parallel Compilation has detected 8 hyper-threaded processors. However, the extra hyper-threaded processors will not be used by default. Parallel Compilation will use 4 of th
- 12021 Found 2 design units, including 1 entities, in source file partial_full_adder.vhd
- 12127 Elaborating entity "partial_full_adder" for the top level hierarchy
- 286030 Timing-Driven Synthesis is running
- 16010 Generating hard_block partition "hard_block:auto_generated_inst"
- 21057 Implemented 9 device resources after synthesis - the final resource count might be different
- Quartus II 64-bit Analysis & Synthesis was successful. 0 errors, 0 warnings

The status bar at the bottom indicates 'System / Processing (10)' and '100% 00:00:04'.


❖ RTL view:

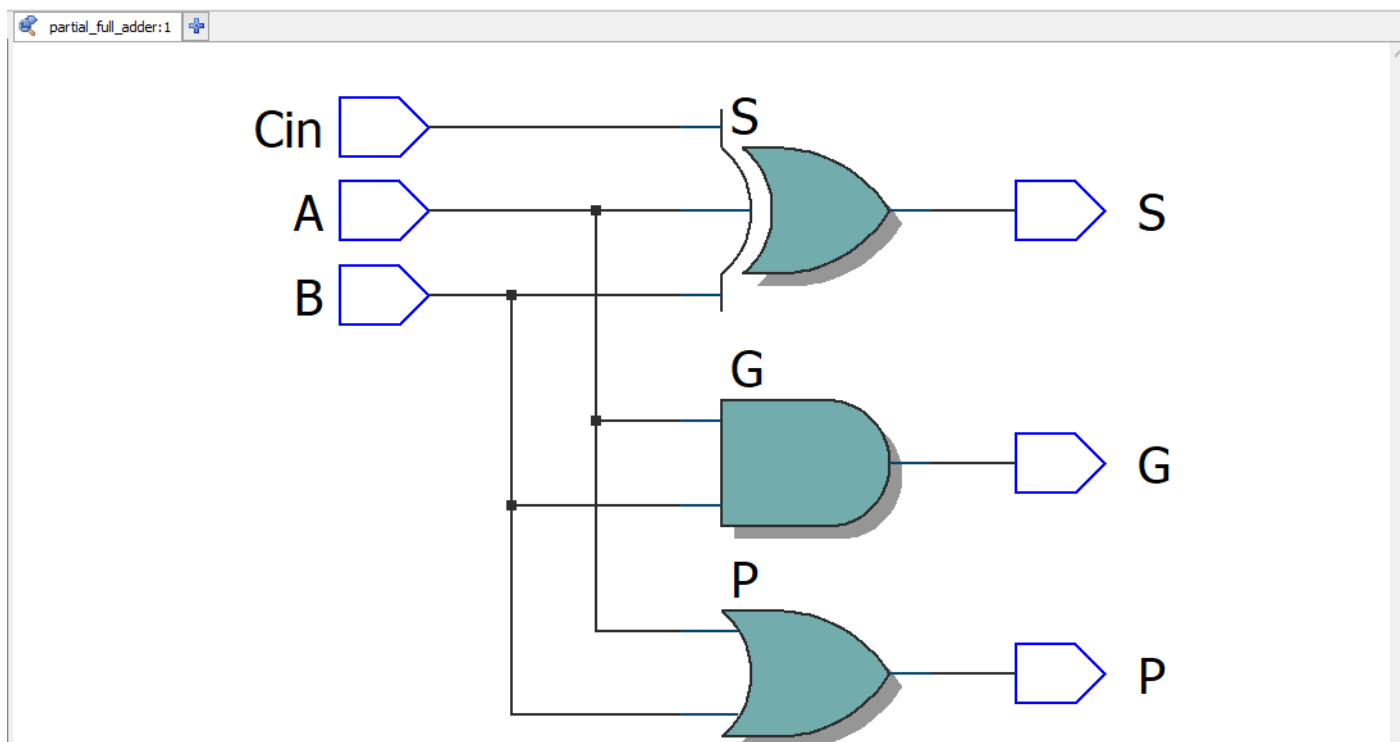

❖ Post-mapping view:

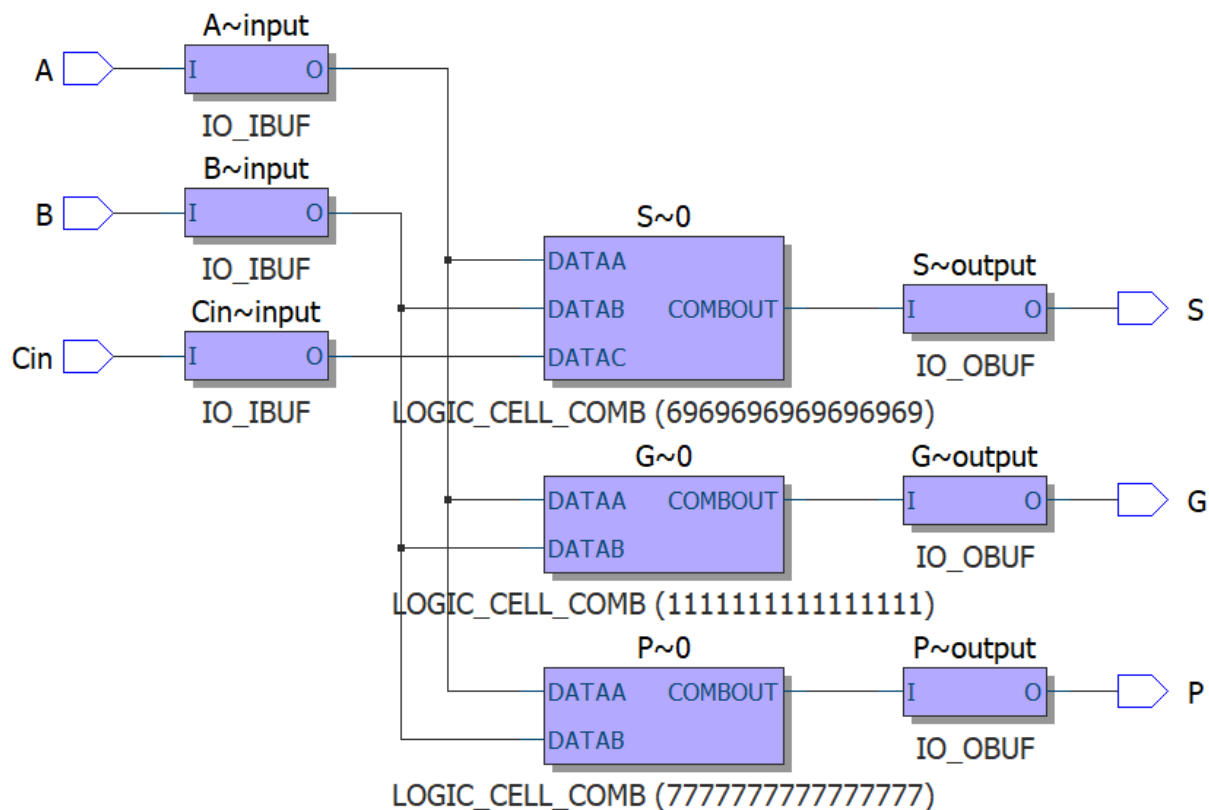

❖ Wave Form:

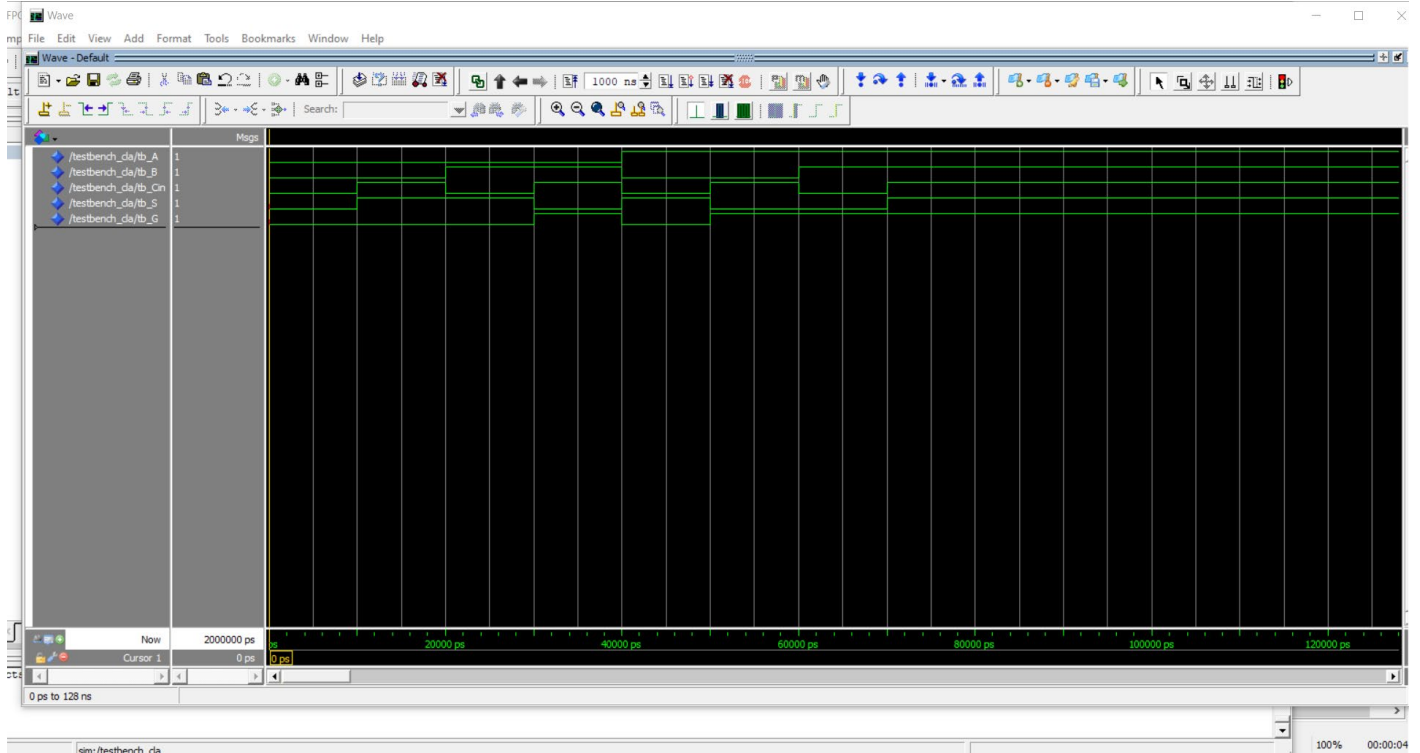

❖ Test bench code:

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- Define the test bench entity

entity TestBench_CLA is

-- Testbench does not have any ports

end TestBench_CLA;

architecture behavior of TestBench_CLA is

-- Component Declaration for the Carry Adder

component carry_adder

Port (

A : in STD_LOGIC;

B : in STD_LOGIC;

```

    Cin : in STD_LOGIC;

    S   : out STD_LOGIC;

    G   : out STD_LOGIC

);

end component;

-- Signals for interfacing with the component
signal tb_A, tb_B, tb_Cin : STD_LOGIC := '0';
signal tb_S, tb_G : STD_LOGIC;

begin

-- Instantiate the Unit Under Test (UUT)
 uut: carry_adder port map (
    A => tb_A,
    B => tb_B,
    Cin => tb_Cin,
    S => tb_S,
    G => tb_G
);

-- Stimulus process
stim_proc: process
begin
    -- Test all input combinations
    tb_A <= '0'; tb_B <= '0'; tb_Cin <= '0';
    wait for 10 ns;

    tb_A <= '0'; tb_B <= '0'; tb_Cin <= '1';
    wait for 10 ns;

    tb_A <= '0'; tb_B <= '1'; tb_Cin <= '0';

```

```
wait for 10 ns;
```

```
tb_A <= '0'; tb_B <= '1'; tb_Cin <= '1';
```

```
wait for 10 ns;
```

```
tb_A <= '1'; tb_B <= '0'; tb_Cin <= '0';
```

```
wait for 10 ns;
```

```
tb_A <= '1'; tb_B <= '0'; tb_Cin <= '1';
```

```
wait for 10 ns;
```

```
tb_A <= '1'; tb_B <= '1'; tb_Cin <= '0';
```

```
wait for 10 ns;
```

```
tb_A <= '1'; tb_B <= '1'; tb_Cin <= '1';
```

```
wait for 10 ns;
```

```
-- Complete the simulation
```

```
wait;
```

```
end process;
```

```
end behavior;
```

Question 2

Q2. For a T flip flop, we the next state of flip flop driven by XOR T (input of circuit) and Q which is the current state of our circuit so based on this and based on t ff truth table I wrote a code for it. First here is a truth table of t ff:

❖ T FF truth table:

Truth table			
CLK	T	Q_{next}	Comment
Rising edge	0	Q	Hold state
Falling edge	0	Q	Hold state
Rising edge	1	\bar{Q}	Toggle
Falling edge	1	Q	No change

Q_{next} - "after the clock transition" output

Q - the current output

❖ Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity tff is
    Port ( clk : in STD_LOGIC;
          async_reset : in STD_LOGIC;
          Q : out STD_LOGIC);
end entity tff;
```



```


architecture toggle of tff is
signal S_Q : std_LOGIC := '0';
begin
    process(clk, async_reset)
    begin
        if async_reset = '1' then
            S_Q <= '0';
        elsif rising_edge(clk) then
            S_Q <= not S_Q;
        end if;
    end process;

    Q <= S_Q;
end architecture toggle;


```

*****: in this code I declared 2 inputs: clk for clock pin of circuit and the async_reset for reset pin of circuit. The output is Q which is next state of circuit. Reset pin Is asynchronous from clock pin and it is active high so it means when pin becomes 1 the output of circuit be 0. I used signals to work with outputs Q because we can not directly work with Q. signal is a wired in VHDL.

❖ Output after compile:

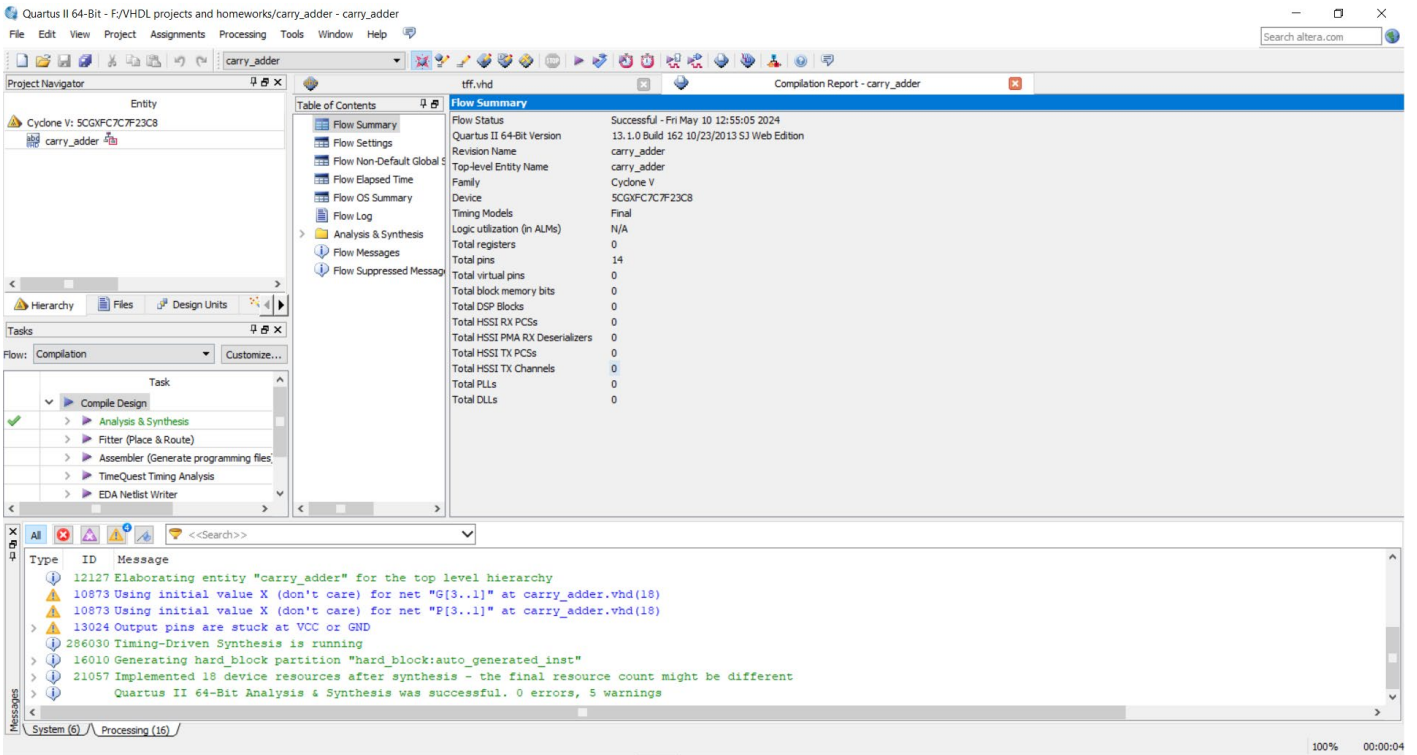


RTL view:

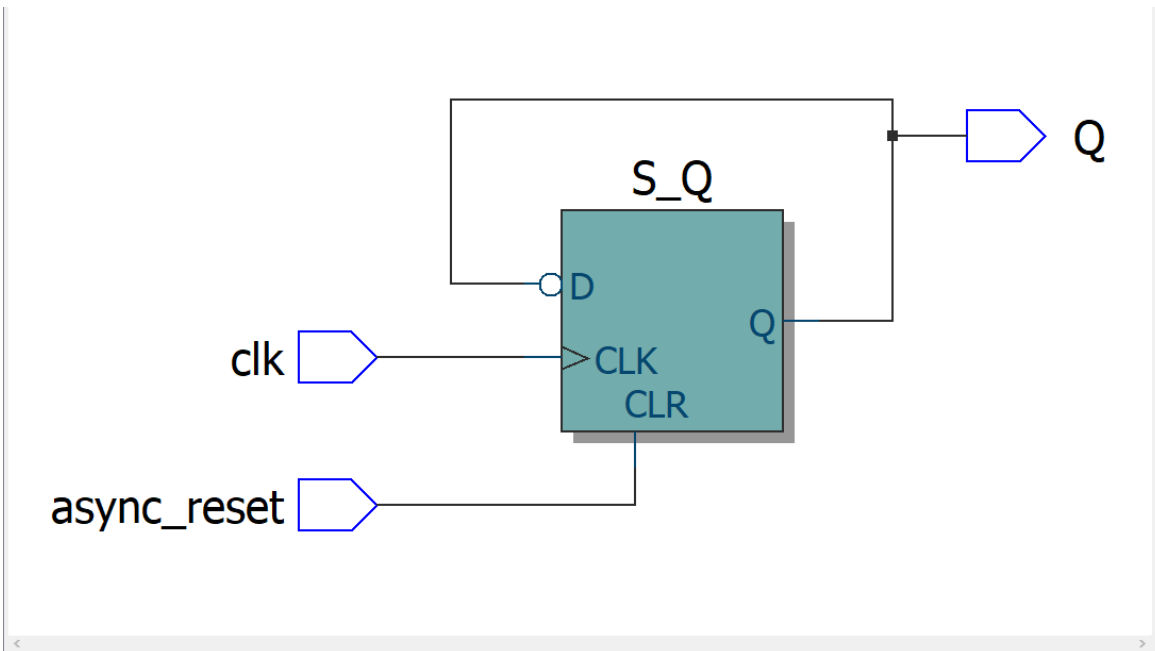


*: notice that in this code we built a T flip flop using D flip flop. This is achieved by feeding the output of the D Flip flop to its input through an XOR gate.

❖ Post-mapping view:

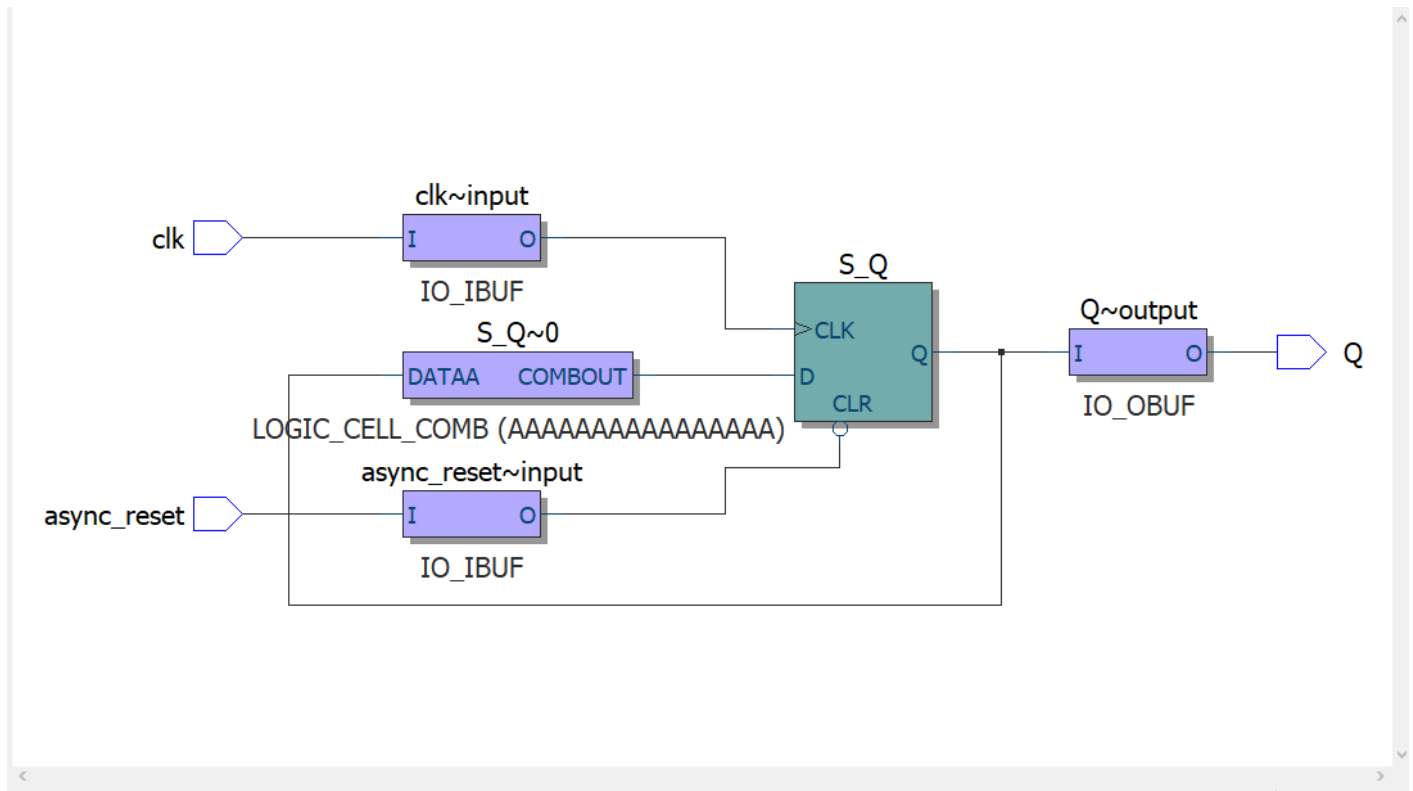

❖ Wave Form:

 

❖ Test bench code:

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity tb_tff is

-- Testbench does not have any ports

end tb_tff;

architecture behavior of tb_tff is

-- Component Declaration for the T Flip-Flop

component tff

Port (clk : in STD_LOGIC;

async_reset : in STD_LOGIC;

Q : out STD_LOGIC);

```
end component;
```

```
-- Signals for interfacing with the component
```

```
signal tb_clk : STD_LOGIC := '0';
```

```
signal tb_reset : STD_LOGIC := '0';
```

```
signal tb_Q : STD_LOGIC;
```

```
-- Clock period definition
```

```
constant clk_period : time := 10 ns;
```

```
begin
```

```
-- Instantiate the T Flip-Flop
```

```
uut: tff port map (
```

```
    clk => tb_clk,
```

```
    async_reset => tb_reset,
```

```
    Q => tb_Q
```

```
);
```

```
-- Clock process definitions
```

```
clk_process : process
```

```
begin
```

```
    while true loop
```

```
        tb_clk <= '0';
```

```
        wait for clk_period/2;
```

```
        tb_clk <= '1';
```

```
        wait for clk_period/2;
```

```
    end loop;
```

```
end process;
```

```
-- Stimulus process
stim_proc: process
begin
    -- Test 1: Reset the flip-flop
    tb_reset <= '1';
    wait for 25 ns;
    tb_reset <= '0';
    wait for 25 ns;

    -- Test 2: Allow some clock pulses to toggle the flip-flop
    tb_reset <= '0';
    wait for 100 ns;

    -- Test 3: Assert reset while clock is running
    tb_reset <= '1';
    wait for 20 ns;
    tb_reset <= '0';
    wait for 100 ns;

    -- End of testing
    wait;
end process;
end behavior;
```

question 3

Q3. Designing a 4-bit BCD (Binary-Coded Decimal) up/down counter in VHDL involves creating a circuit that counts from 0 to 9 and back again, with the count direction controlled by an input signal **Dir**.

❖Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;


entity BCD_Counter is
    Port (
        clk : in STD_LOGIC;
        reset : in STD_LOGIC;
        Dir : in STD_LOGIC; -- '0' for down, '1' for up
        count : out STD_LOGIC_VECTOR(3 downto 0)
    );
end BCD_Counter;

architecture Behavioral of BCD_Counter is
    signal r_count : STD_LOGIC_VECTOR(3 downto 0) := "0000";
begin
    process(clk, reset)
    begin
        if reset = '1' then
            r_count <= "0000"; -- Reset the counter
        elsif rising_edge(clk) then
            if Dir = '1' then -- Count up
```


```
    if r_count = "1001" then -- Max value for BCD
        r_count <= "0000"; -- Wrap around
    else
        r_count <= r_count + 1;
    end if;
else -- Count down
    if r_count = "0000" then
        r_count <= "1001"; -- Wrap around from 0 to 9
    else
        r_count <= r_count - 1;
    end if;
end if;
end if;
end process;

count <= r_count; -- Output the current count
end Behavioral;
```

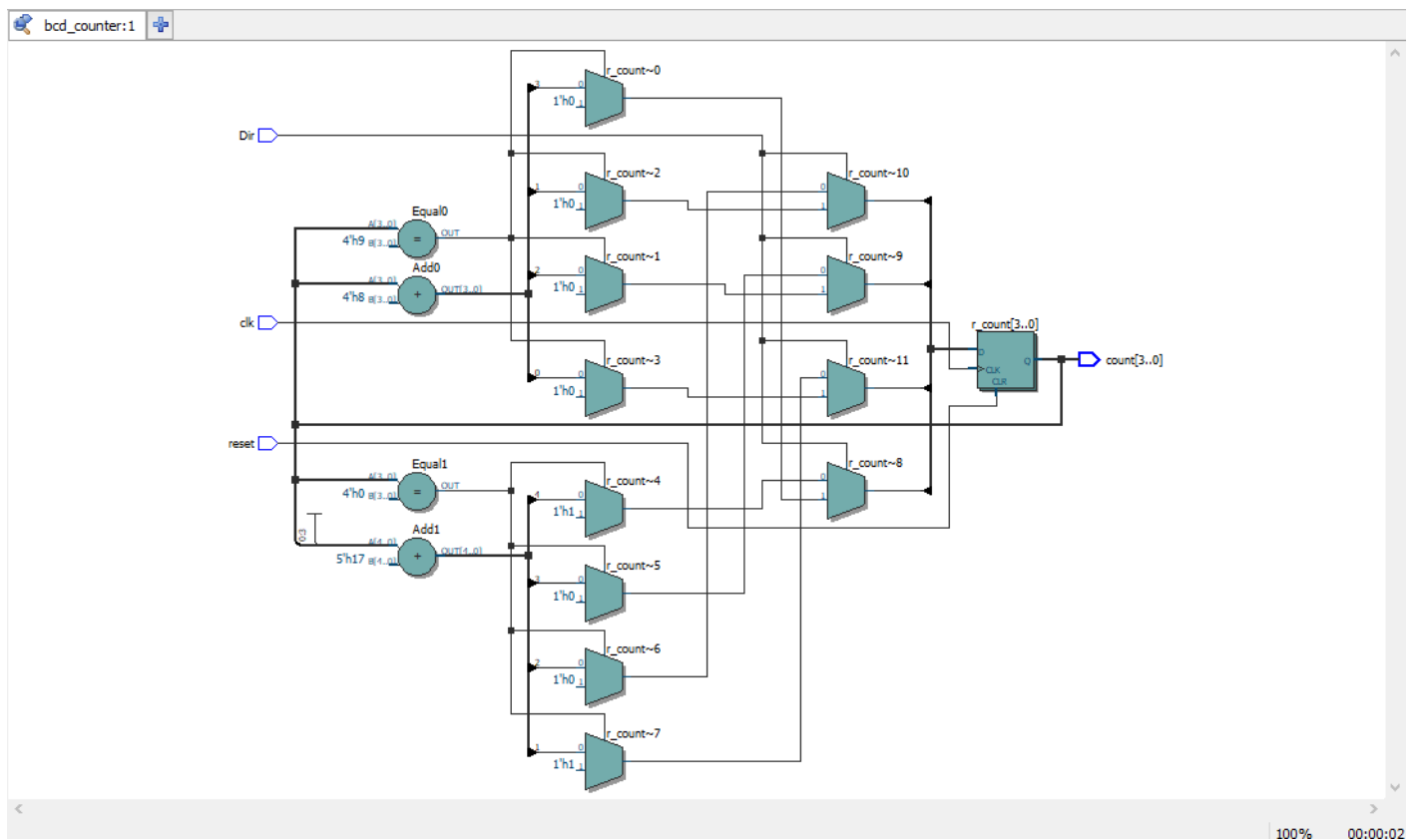

Quartus II 64-Bit - F:/VHDL projects and homeworks/bcd_counter - bcd_counter



❖ Post-mapping view:

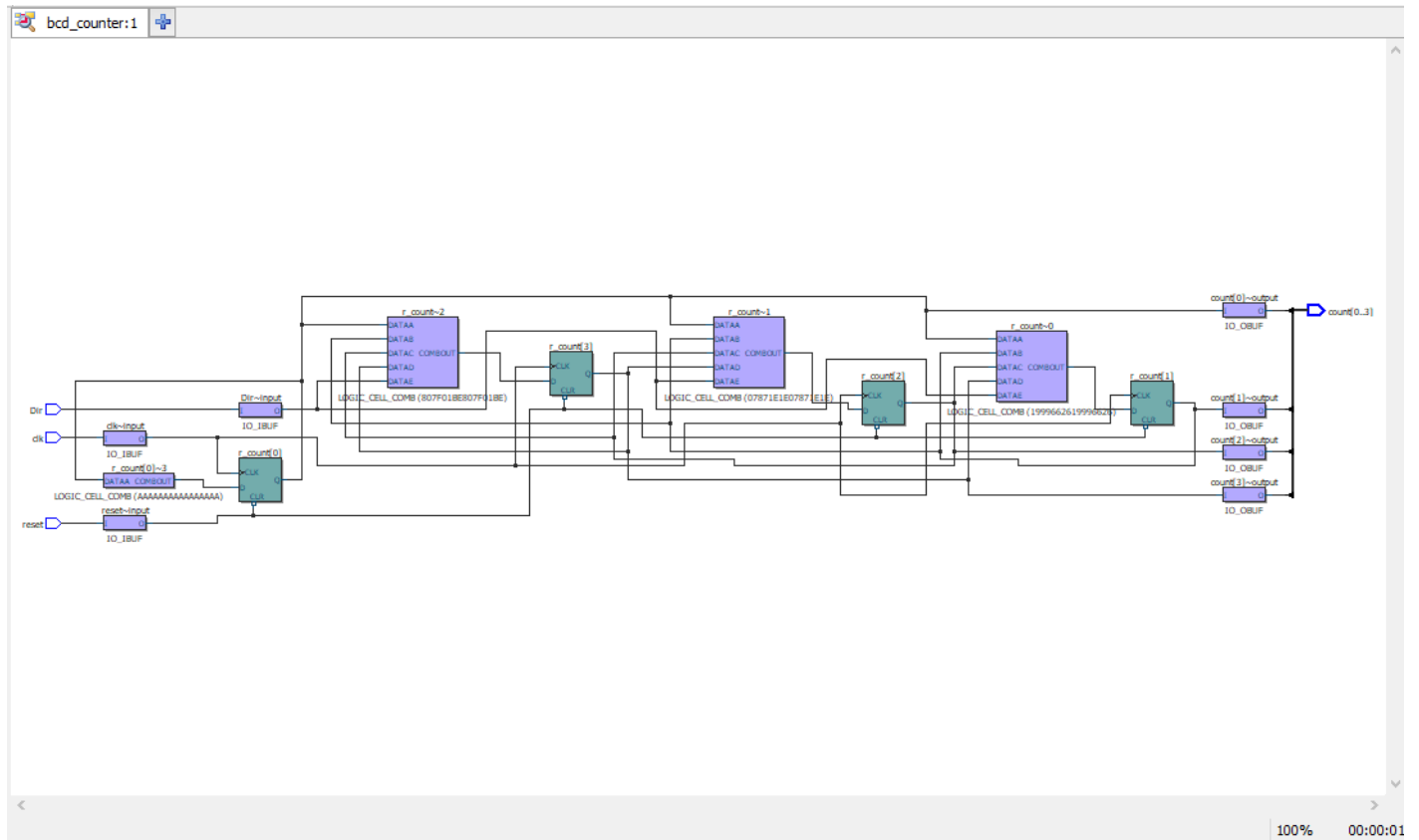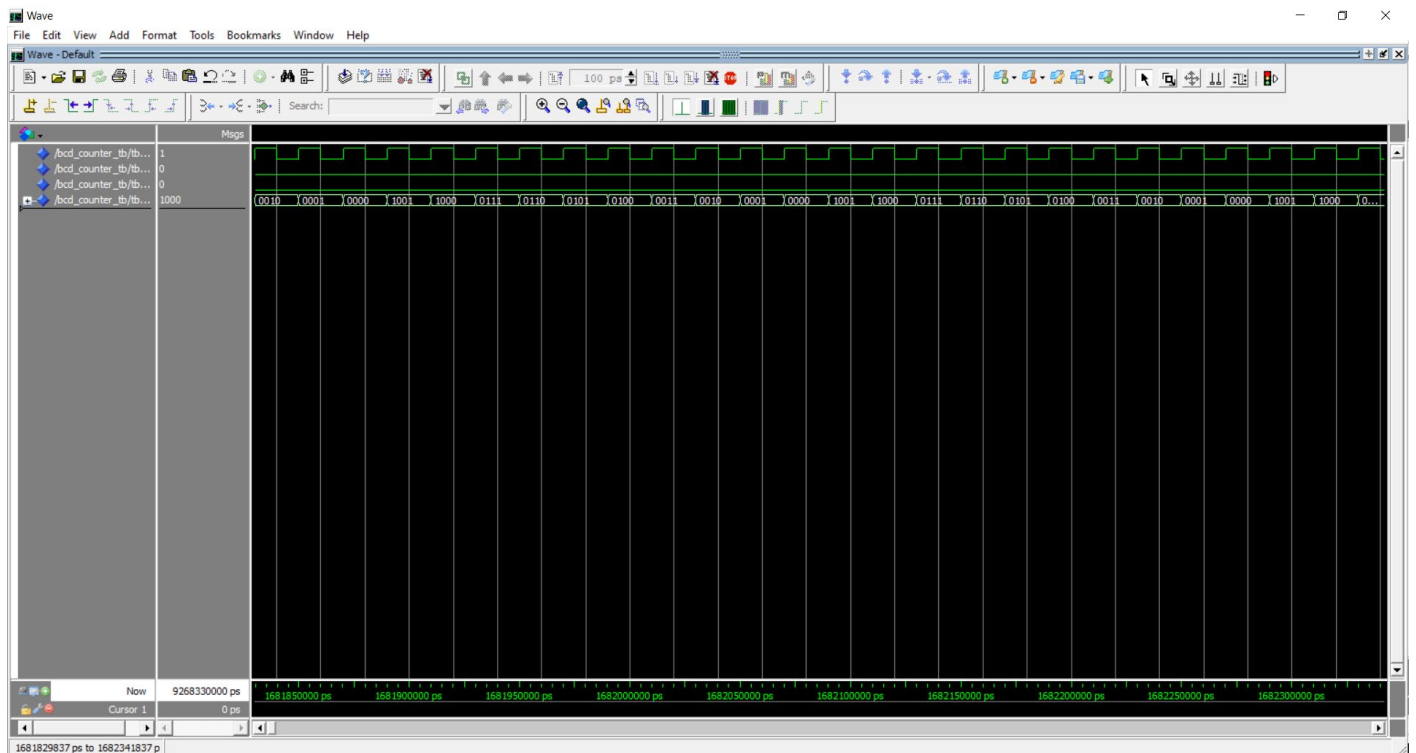

❖ Wave form:



❖ Test bench code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity BCD_Counter_TB is
-- Testbench has no ports
end BCD_Counter_TB;

architecture behavior of BCD_Counter_TB is
-- Component Declaration
component BCD_Counter
Port (
    clk : in STD_LOGIC;
    reset : in STD_LOGIC;
    Dir : in STD_LOGIC;
    count : out STD_LOGIC_VECTOR(3 downto 0));
end component;

-- Test Signals
signal tb_clk : STD_LOGIC := '0';
signal tb_reset : STD_LOGIC := '0';
signal tb_Dir : STD_LOGIC := '0';
signal tb_count : STD_LOGIC_VECTOR(3 downto 0);

begin
-- Clock process
clk_process : process
```

```

begin
    tb_clk <= '0';
    wait for 10 ns; -- Clock period of 20 ns
    tb_clk <= '1';
    wait for 10 ns;
end process;

-- Instantiate the Unit Under Test (UUT)
 uut: BCD_Counter port map (
    clk => tb_clk,
    reset => tb_reset,
    Dir => tb_Dir,
    count => tb_count);

-- Test Stimulus Process
stim_proc: process
begin
    -- Initialize Inputs
    tb_reset <= '1'; -- Assert reset initially
    wait for 40 ns;
    tb_reset <= '0'; -- De-assert reset
    wait for 20 ns;

    -- Test Count Up
    tb_Dir <= '1'; -- Set direction to up
    wait for 220 ns; -- Allow enough time to observe the count

    -- Test Count Down

```

```
tb_Dir <= '0'; -- Change direction to down
wait for 220 ns; -- Allow enough time to observe the count

-- Finish simulation
wait;
end process;

end behavior;
```

Question 4

Q4. to write a VHDL code that implement pattern transformation for the given table I'll create a state machine where each state corresponds to one of the input patterns and transition to the corresponding next pattern.

❖Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Define the entity for the pattern transformation
entity Pattern_Finder is
    Port (
```

```

    clk : in STD_LOGIC;
    reset : in STD_LOGIC;
    input_pattern : in STD_LOGIC_VECTOR(2 downto 0);
    next_pattern : out STD_LOGIC_VECTOR(2 downto 0)
);
end Pattern_Finder;

-- Architecture declaration using a behavioral model
architecture Behavioral of Pattern_Finder is
    signal current_state, next_state : STD_LOGIC_VECTOR(2 downto 0);
begin

    -- State register process
    process(clk, reset)
    begin
        if reset = '1' then
            current_state <= "000"; -- Default state
        elsif rising_edge(clk) then
            current_state <= next_state;
        end if;
    end process;

    -- Next state logic based on current state
    process(current_state)
    begin
        case current_state is
            when "000" => next_state <= "011";
            when "011" => next_state <= "110";
            when "110" => next_state <= "101";

```


```
next_pattern <= next_state; -- Directly map next state to output
```

end Behavioral;


❖ output after compilation:

[illegible]


❖ RTL view:

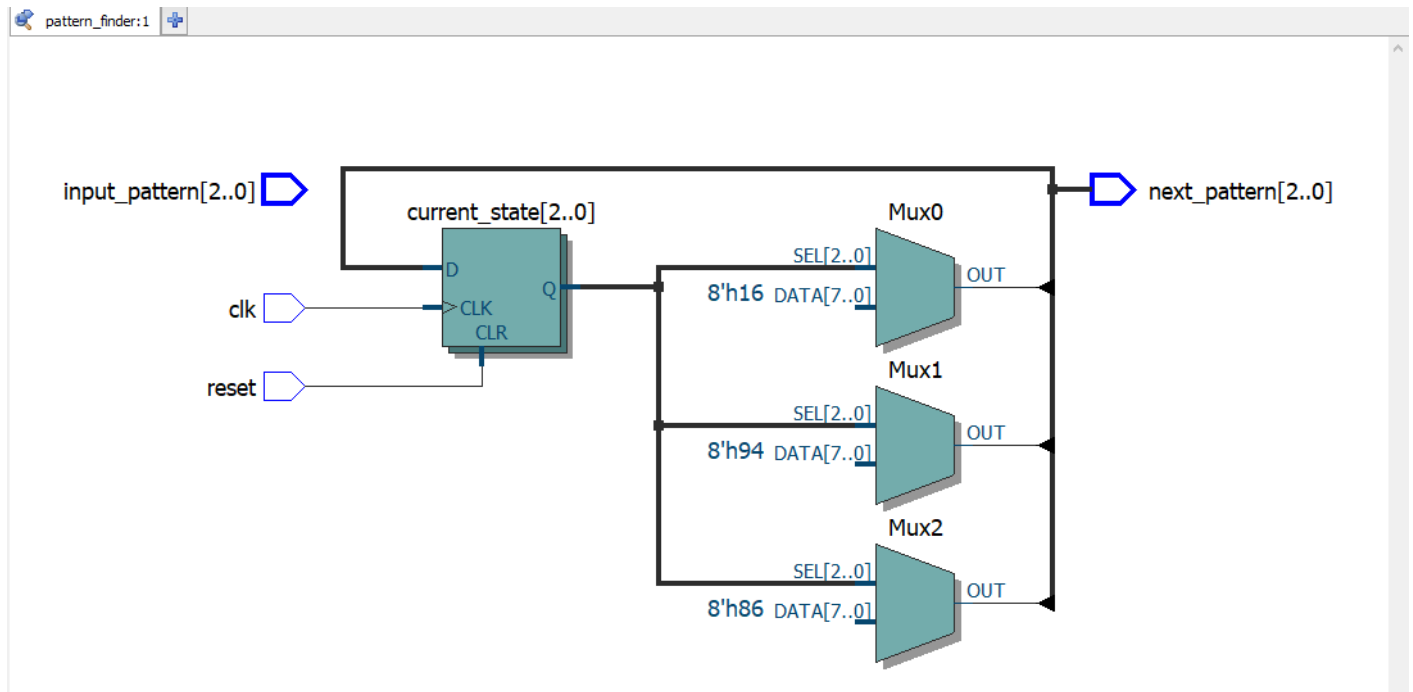

❖ Post-mapping view:

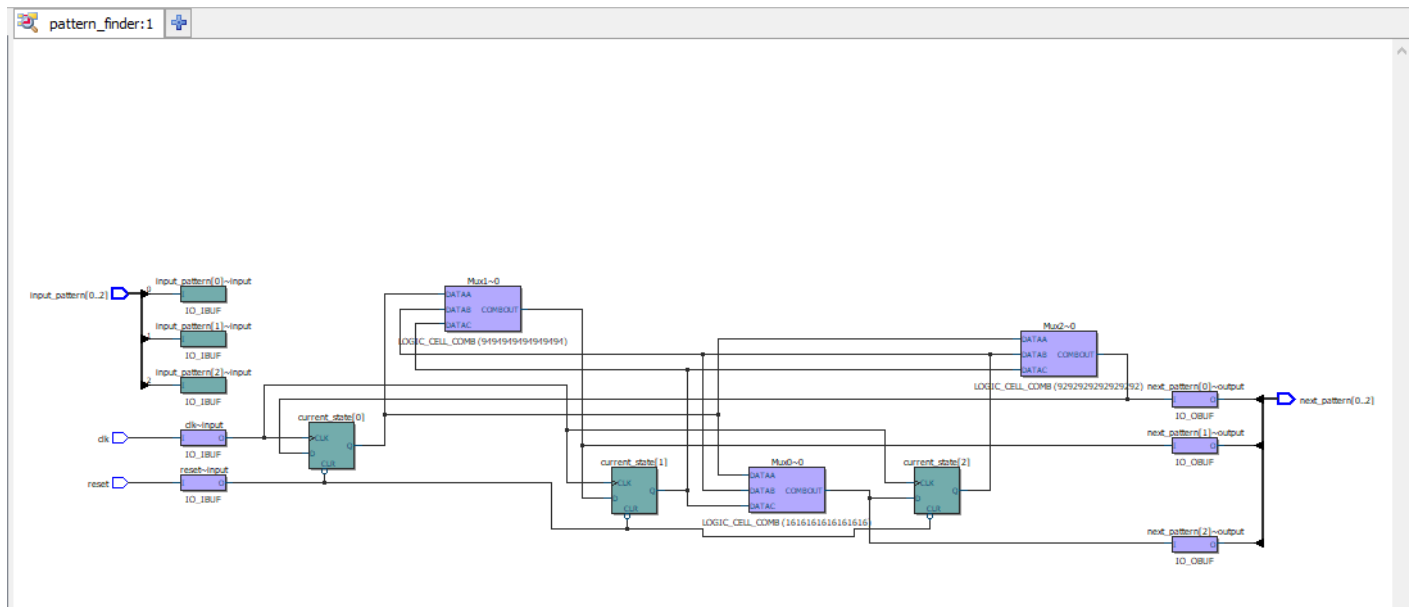

❖ Wave form:

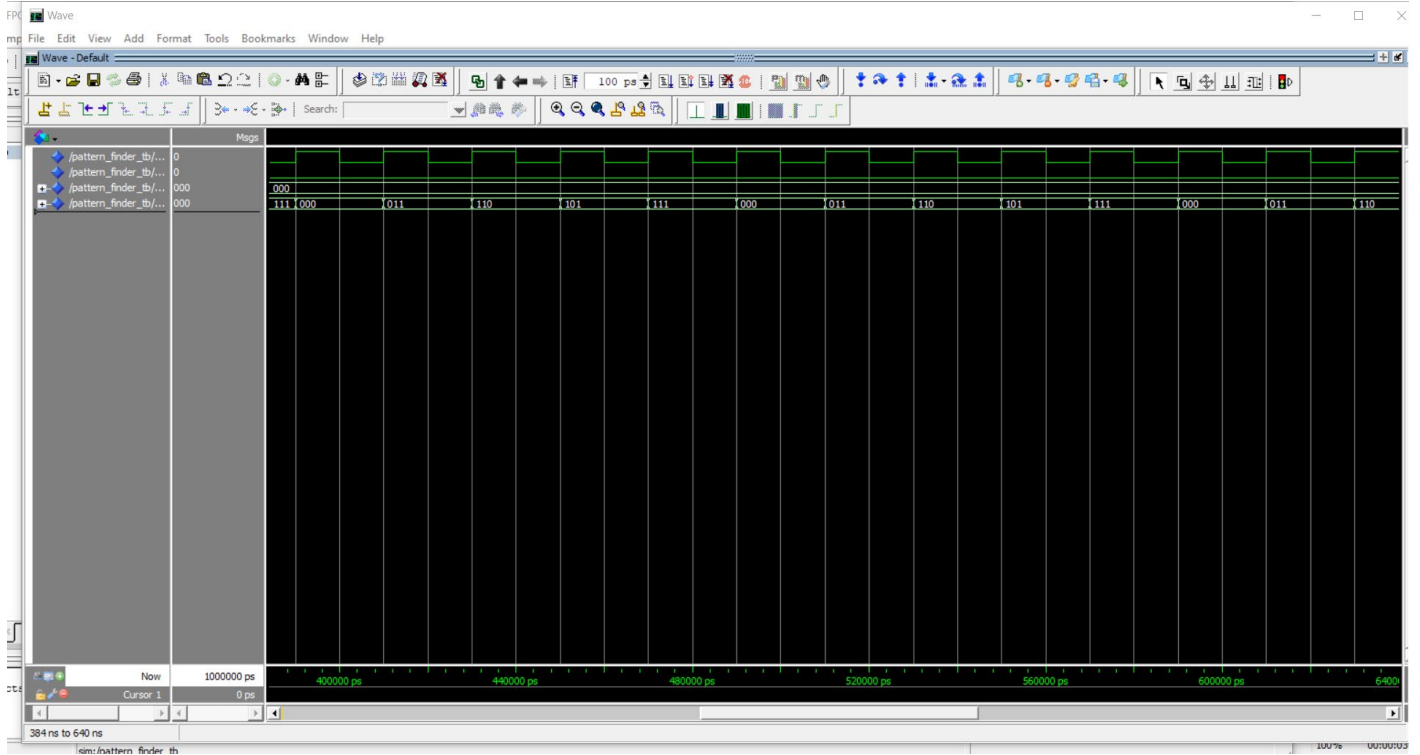

❖ Test bench code:

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Define the test bench entity
```

```
entity Pattern_Finder_TB is
```

```
-- Testbench does not have any ports
```

```
end Pattern_Finder_TB;
```

```
architecture behavior of Pattern_Finder_TB is
```

```
-- Component Declaration for the Pattern_Finder
```

```
component Pattern_Finder
```

```
Port (
```

```
    clk : in STD_LOGIC;
```

```
    reset : in STD_LOGIC;
```

```

    input_pattern : in STD_LOGIC_VECTOR(2 downto 0);
    next_pattern : out STD_LOGIC_VECTOR(2 downto 0)
);
end component;

-- Signals for interfacing with the component
signal tb_clk : STD_LOGIC := '0';
signal tb_reset : STD_LOGIC := '0';
signal tb_input_pattern : STD_LOGIC_VECTOR(2 downto 0) := (others => '0');
signal tb_next_pattern : STD_LOGIC_VECTOR(2 downto 0);

begin

    -- Clock process
    clk_process: process
    begin
        while true loop
            tb_clk <= '0';

            wait for 10 ns; -- Clock period is 20 ns

            tb_clk <= '1';

            wait for 10 ns;

        end loop;
    end process;

    -- Instantiate the Unit Under Test (UUT)
    uut: Pattern_Finder port map (
        clk => tb_clk,
        reset => tb_reset,
        input_pattern => tb_input_pattern,
        next_pattern => tb_next_pattern
    );
end;

```

```

);

-- Stimulus process
stim_proc: process
begin
    -- Reset the device
    tb_reset <= '1';
    wait for 25 ns; -- wait more than one clock cycle
    tb_reset <= '0';
    wait for 15 ns;

    -- Loop through pattern states
    tb_input_pattern <= "000"; -- Start at pattern "000"
    wait for 20 ns; -- wait for one cycle
    tb_input_pattern <= "011";
    wait for 20 ns;
    tb_input_pattern <= "110";
    wait for 20 ns;
    tb_input_pattern <= "101";
    wait for 20 ns;
    tb_input_pattern <= "111";
    wait for 20 ns;
    tb_input_pattern <= "000"; -- Wrap around
    wait for 20 ns;

    -- Finish the simulation
    wait;
end process;
end behavior;

```

